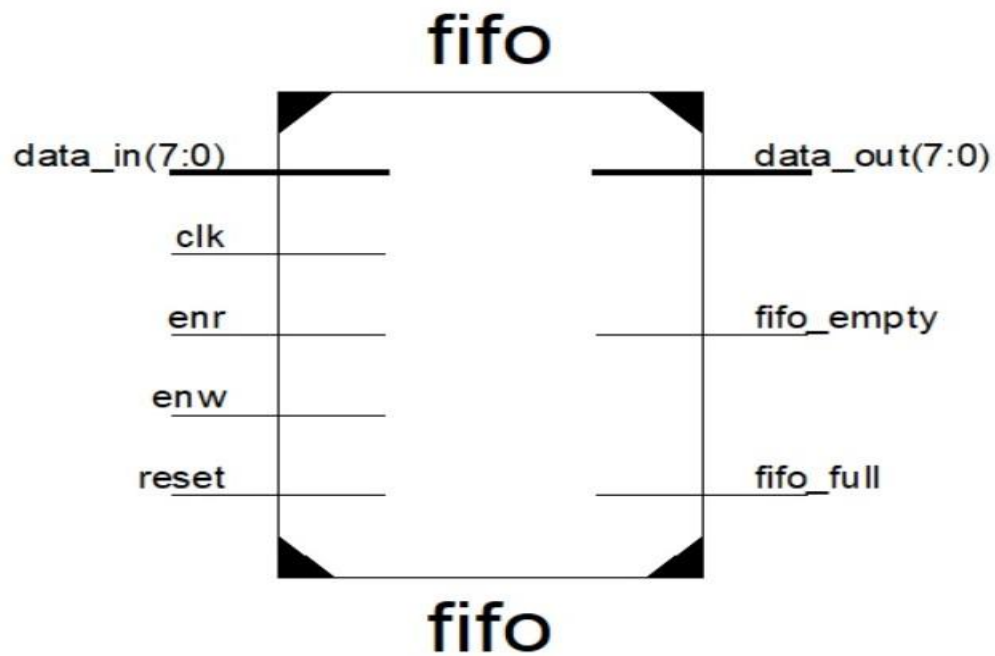


Class	:	
Batch	:	
ABC ID	:	
Roll. No	:	
Assignment No.	:	A.4
Assignment Name	:	FIFO (32-bit , organized as 4 X 8 , BYTE Addressable)
Date Of Performance	:	

BLOCK DIAGRAM



FUNCTION TABLE

reset	clk	enw	enr	data_out	fifo_empty	fifo_full
1	x	x	x	(00) ₁₆	1	0
0	↓	1	0	NA	0	0
0	↓	1	0	NA	0	0
0	↓	1	0	NA	0	0
0	↓	1	0	NA	0	1
0	↓	0	1	mem ₀	0	0
0	↓	0	1	mem ₁	0	0
0	↓	0	1	mem ₂	0	0
0	↓	0	1	mem ₃	0	0

MAIN VHDL MODEL (MVM)

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity fifo is
generic (depth : integer := 16); --depth of fifo
port ( clk : in std_logic;
      reset : in std_logic;
      enr : in std_logic; --enable read,should be '0' when not in use.
      enw : in std_logic; --enable write,should be '0' when not in use.
      data_in : in std_logic_vector (7 downto 0); --input data
      data_out : out std_logic_vector(7 downto 0); --output data
      fifo_empty : out std_logic; --set as '1' when the queue is empty
      fifo_full : out std_logic --set as '1' when the queue is full
    );
end fifo;

architecture fifo_arch of fifo is

type memory_type is array (0 to depth-1) of std_logic_vector(7 downto 0);
signal memory : memory_type :=(others => (others => '0')); --memory for queue.
signal readptr,writeptr : integer := 0; --read and write pointers.
signal empty,full : std_logic := '0';

begin

fifo_empty <= empty;
fifo_full <= full;

process(Clk,reset)
--this is the number of elements stored in fifo at a time.
--this variable is used to decide whether the fifo is empty or full.
variable num_elem : integer := 0;
begin
if(reset = '1') then

-- for i in 0 to depth-1 loop
--
--      memory(i)<=(others=>'0');
--      end loop;
memory <= (others => (others=> '0'));

data_out <= (others => '0');
empty <= '1';
full <= '0';
readptr <= 0;
writeptr <= 0;
num_elem := 0;
elsif(rising_edge(Clk)) then
if(enr = '1' and empty = '0') then --read
```


```



    data_out <= memory(readptr);
    readptr <= readptr + 1;
    num_elem := num_elem-1;
end if;
if(enw = '1' and full = '0') then  --write
    memory(writeptr) <= data_in;
    writeptr <= writeptr + 1;
    num_elem := num_elem+1;
end if;
--rolling over of the indices.
if(readptr = depth-1) then  --resetting read pointer.
    readptr <= 0;
end if;
if(writeptr = depth-1) then  --resetting write pointer.
    writeptr <= 0;
end if;
--setting empty and full flags.
if(num_elem = 0) then
    empty <= '1';
else
    empty <= '0';
end if;
if(num_elem = depth) then
    full <= '1';
else
    full <= '0';
end if;
end if;
end process;

end fifo_arch;


```

RTL SCHEMATIC:

 

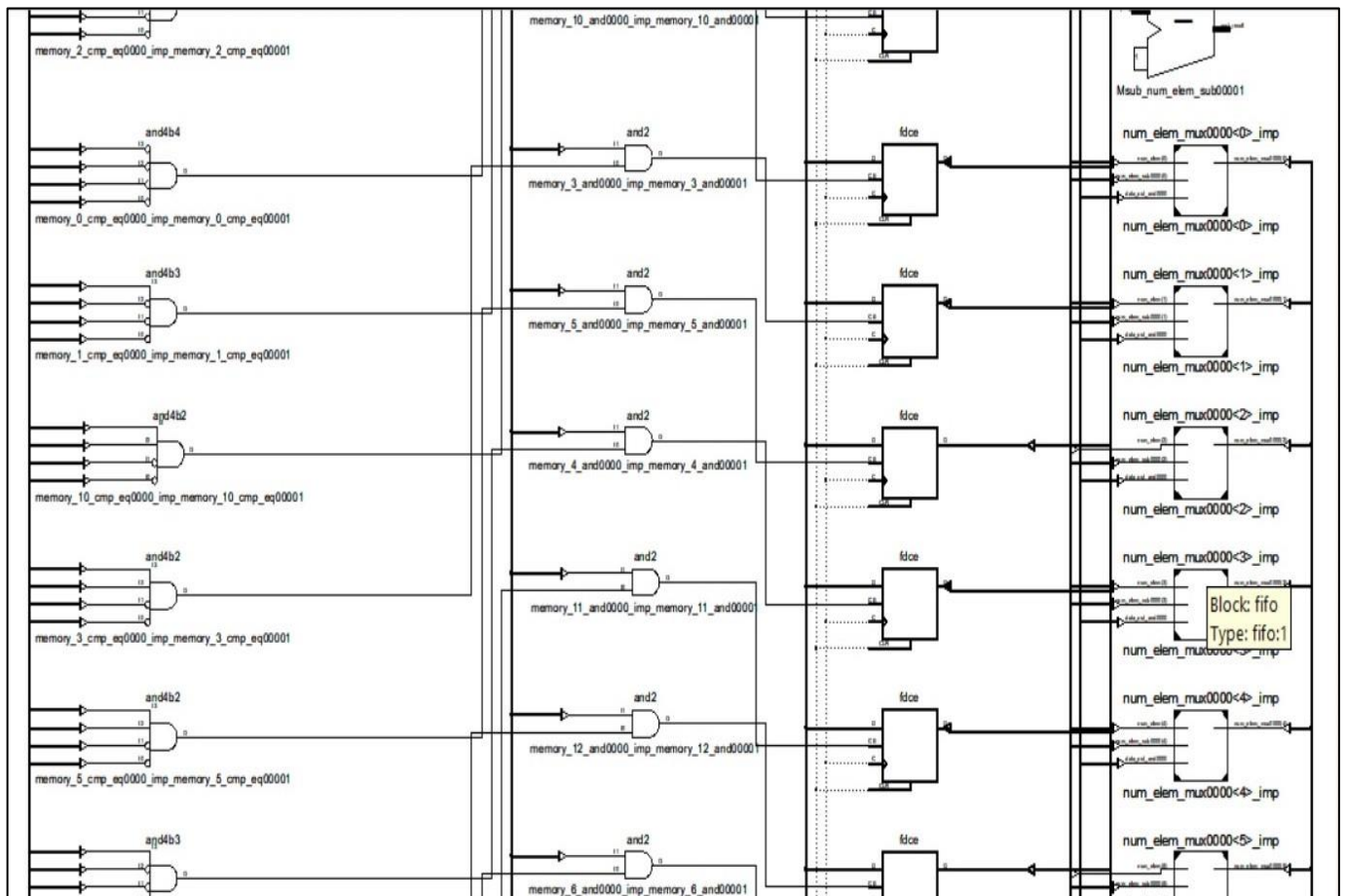 

TECHNOLOGY SCHEMATIC

 

SYNTHESIS REPORT

a) Device Utilization Summary:

```
=====
*                      Final Report                      *
=====

Final Results
RTL Top Level Output File Name  : FIFO_4x8.ngr
Top Level Output File Name     : FIFO_4x8
Output Format                   : NGC
Optimization Goal               : Speed
Keep Hierarchy                 : No

Design Statistics
# IOs                          : 23

Cell Usage :
# BELS                : 32
#  GND                : 1
#  INV                : 2
#  LUT3               : 21
#  MUXF5              : 8
# FlipFlops/Latches   : 42
#  FDC_1              : 1
#  FDCE_1             : 40
#  FDP_1              : 1
# Clock Buffers       : 1
#  BUFGP              : 1
# IO Buffers          : 22
#  IBUF               : 12
#  OBUF               : 10
=====
```

Device utilization summary:

Selected Device : 3s250epq208-5

Number of Slices:	26 out of 2448	1%
Number of Slice Flip Flops:	40 out of 4896	0%
Number of 4 input LUTs:	23 out of 4896	0%
Number of IOs:	23	
Number of bonded IOBs:	23 out of 158	14%
IOB Flip Flops:	2	
Number of GCLKs:	1 out of 24	4%

b) TIMING REPORT:

NOTE: THESE TIMING NUMBERS ARE ONLY A SYNTHESIS ESTIMATE.
FOR ACCURATE TIMING INFORMATION PLEASE REFER TO THE TRACE REPORT

GENERATED AFTER PLACE-and-ROUTE.

Clock Information:

-----+			
Clock Signal	Clock buffer(FF name)	Load	
-----+			
clk	BUFGP	42	
-----+			

Asynchronous Control Signals Information:

-----+			
Control Signal	Buffer(FF name)	Load	
-----+			
rst_inv(rst_inv1_INV_0:O)	NONE(d_out_0)	42	
-----+			

Timing Summary:

Speed Grade: -5

Minimum period: 2.098ns (Maximum Frequency: 476.644MHz)
Minimum input arrival time before clock: 3.955ns
Maximum output required time after clock: 4.040ns
Maximum combinational path delay: No path found

Timing Detail:

All values displayed in nanoseconds (ns)

TESTBENCH VHDL MODEL (TVM)

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.std_logic_arith.ALL;

ENTITY fifo_tb IS
END fifo_tb;

ARCHITECTURE behavior OF fifo_tb IS
    --Inputs and outputs
    signal Clk,reset,enr,enw,empty,full : std_logic := '0';
    signal data_in,data_out : std_logic_vector(7 downto 0) := (others => '0');
    --temporary signals
    signal i : integer := 0;
    -- Clock period definitions
    constant Clk_period : time := 10 ns;
    constant depth : integer := 16; --specify depth of fifo here.

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: entity work.fifo generic map(depth => depth) PORT MAP
    (clk,reset,enr,enw,data_in,data_out,empty,full);

    -- Clock process definitions
    Clk_process :process
    begin
        Clk <= '0';
        wait for Clk_period/2;
        Clk <= '1';
        wait for Clk_period/2;
    end process;

    -- Stimulus process
    stim_proc: process
    begin
        reset <= '1'; --apply reset for one clock cycle.
        wait for clk_period;
        reset <= '0';
        wait for clk_period*3; --wait for 3 clock periods(simply)
        enw <= '1';  enr <= '0';    --write 10 values to fifo.
        for i in 1 to 10 loop
            Data_In <= conv_std_logic_vector(i,8);
            wait for clk_period;
        end loop;
        enw <= '0';  enr <= '1';    --read 4 values from fifo.
        wait for clk_period*4;
        enw <= '0';  enr <= '0';
        wait for clk_period*10; --wait for some clock cycles.
```


```

    enw <= '1';  enr <= '0';    --write 10 values to fifo.
for i in 11 to 20 loop
    Data_In <= conv_std_logic_vector(i,8);
    wait for clk_period;
end loop;
    enw <= '0';  enr <= '0';
    wait for clk_period*10; --wait for some clock cycles.
    enw <= '0';  enr <= '1';    --read 4 values from fifo.
wait for clk_period*4;
    enw <= '0';  enr <= '0';
    wait for clk_period;
    enw <= '0';  enr <= '1';    --read 4 values from fifo.
wait for clk_period*8;
    enw <= '0';  enr <= '0';
    wait for clk_period;
    enw <= '0';  enr <= '1';    --read 8 values from fifo.
wait for clk_period*4;
    enw <= '0';  enr <= '0';
    wait for clk_period;
    enw <= '0';  enr <= '1';    --read 4 values from fifo.
wait for clk_period*4;
    enw <= '0';  enr <= '0';
    wait;
end process;

END;

```

ISIM WAVEFORMS

 

PIN-LOCKING REPORT

PlanAhead Generated physical constraints

```
NET "data_in[7]" LOC = P165;    #sw4-0
NET "data_in[6]" LOC = P167;    #sw4-1
NET "data_in[5]" LOC = P163;    #sw4-2
NET "data_in[4]" LOC = P164;
NET "data_in[3]" LOC = P161;
NET "data_in[2]" LOC = P162;
NET "data_in[1]" LOC = P160;
NET "data_in[0]" LOC = P153;    #sw4-7
NET "data_out[7]" LOC = P179;    #sw3-0
NET "data_out[6]" LOC = P180;    #sw3-1
NET "data_out[5]" LOC = P177;
NET "data_out[4]" LOC = P178;
NET "data_out[3]" LOC = P152;
NET "data_out[2]" LOC = P168;
NET "data_out[1]" LOC = P171;
NET "data_out[0]" LOC = P172;    #sw3-7
NET "clk" LOC = P132;
NET "reset" LOC = P204;         #k0
NET "enr" LOC = P184;           #sw2-6
NET "enw" LOC = P194;           #sw2-7
NET "fifo_empty" LOC = P199;    #sw1-6
NET "fifo_full" LOC = P196;     #sw1-7
```

CONCLUSION

Thus, we have:

- 1) Modeled a 4x8 FIFO using Behavioral Modeling Style.
- 2) Observed following Schematics: **RTL & Technology Schematics** generated **Post-Synthesis**.
- 3) Interpreted **Device Utilization Summary** in terms of LUTs, SLICES, IOBs, Multiplexers & D FFs used out of the available device resources.
- 4) Interpreted the TIMING Report in terms of Maximum combinational delay as indicative of the Maximum Operating Frequency.
- 5) Written a TESTBENCH to verify the functionality of 4x8 FIFO & verified the functionality as per the FUNCTION-TABLE, by observing ISIM Waveforms.
- 6) Used PlanAhead Editor for pin-locking.
- 7) Prototyped the FPGA **XC3S250EPQ208-5** to realize 4x8 FIFO & verified its operation by giving suitable input combinations.